

# Common Misconceptions and Mistakes for Exam 2

Giannacco

Power Generated is associated with delivery, Power Developed is associated with absorption.

$V_{th}$  is an open circuit voltage.  $V_{th} = V_{ab}$ .

$I_N$  is a short circuit current.  $I_N = I_{ab}$ .

Using the test source method to find  $R_{eq}$ , all independent sources are switched off and all dependent sources stay on.

If a named current associated with a dependent source is eliminated *from turning off sources*, the dependent source's value will be zero.

A named current that was discovered BEFORE applying the test-source method does not hold after placing a test source and turning off independent sources.

If a Thevenin or Norton circuit has no independent sources,  $V_{th}$  or  $I_N$  will be zero. This is NOT true if there is an independent current source without an independent voltage source, there will still be voltage.