

For the circuit shown below:

- Find  $I_y$
- Find  $R_x$
- Calculate the power of the unknown element. State whether the power is absorbed or delivered by the unknown element.

