

For the circuit shown below:

- Find the Thevenin equivalent circuit seen from points A and B.
- If a load is connected to points A and B, what is the maximum power that can be delivered to the load?

