

For the circuit below:

- Find the average power P . Determine whether the power is absorbed or delivered.
- Find the reactive power Q . Determine whether the power is absorbed or delivered.
- Write an expression for the sum of average power (ΣP) and reactive power (ΣQ) for every element to check the balance between absorbed and delivered power.

