

For the circuit shown below, find the equivalent resistance seen between points A and B.

