

For the circuit shown below, use the principle of superposition to find I_o . Clearly redraw the circuit.

