

For the circuit shown below, use mesh analysis to generate a system of equations for the circuit. You do not have to solve the generated system of equations.

