

For the steady-state circuit shown below:

- Find voltages V_1 and V_2
- Find currents I_3 and I_4
- Find the energy stored in the capacitor and inductor

