

For the circuit shown below:

- Find the Initial Current $I_L(0)$
- Find an expression for the inductor current $I_L(t)$ for $t \geq 0^+$
- Find an expression for the resistor current $I_o(t)$ for $t \geq 0^+$

