

For the circuit shown below:

- The phasor equivalent for $v_s(t)$ in polar form
- The equivalent impedance seen by the source in both rectangular and polar form
- The steady-state current $i_s(t)$

