
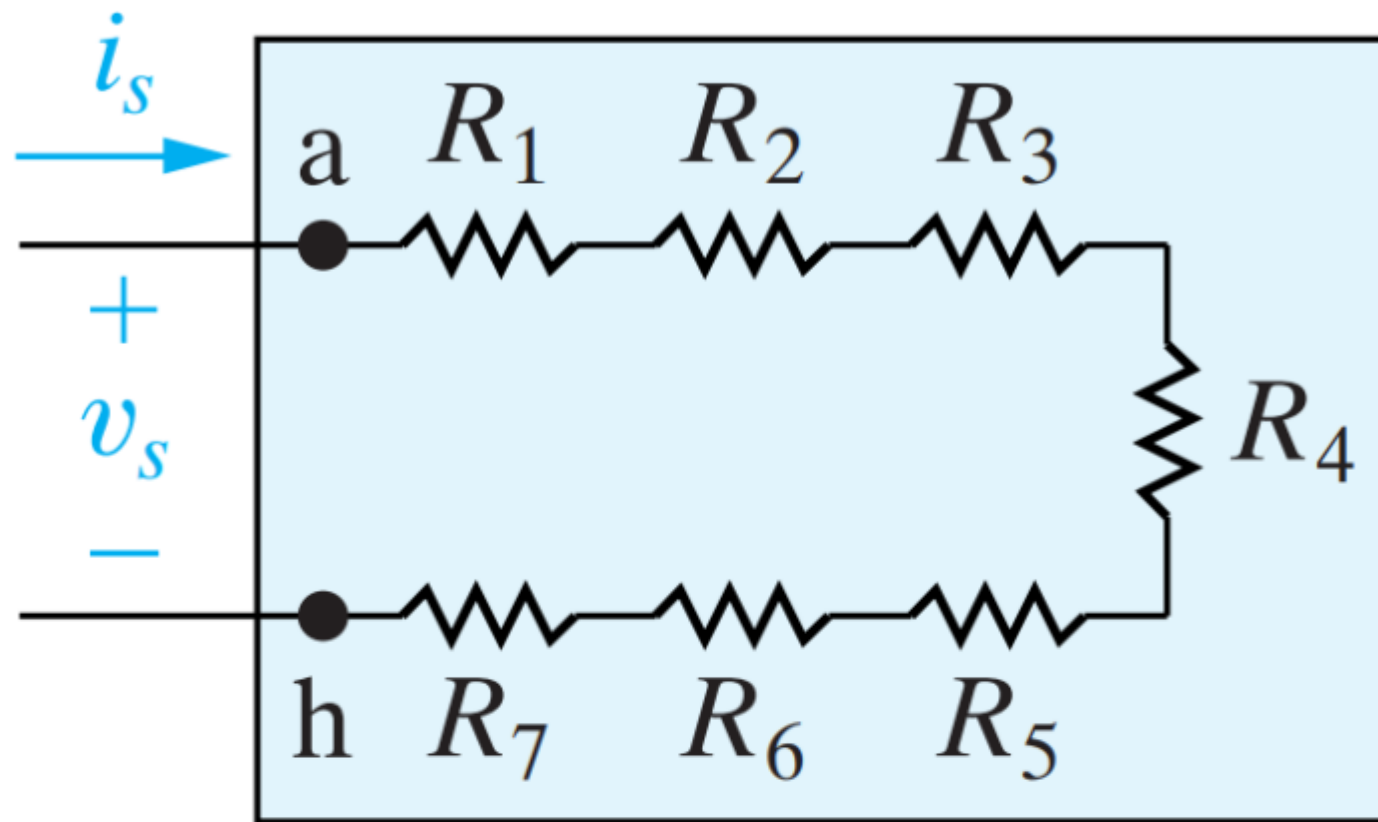


Resistors in Series and Parallel

Series

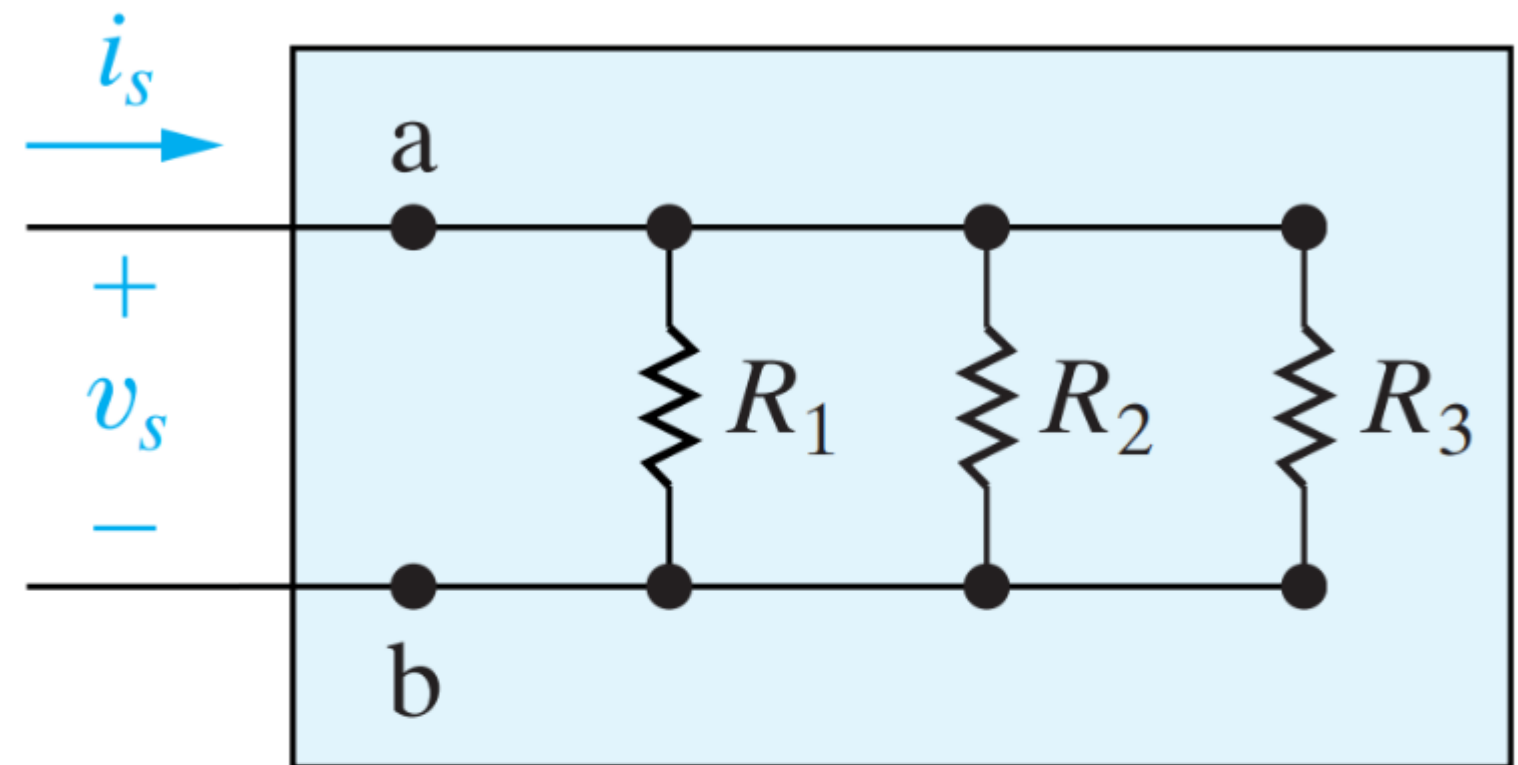

Parallel



Both circuits above can be simplified to a circuit with one equivalent resistor

