

RL/RC Switch Guide

Giannacco

$t = 0$



$t = 0^-$

The switch is closed

$t \geq 0^+$

The switch is open