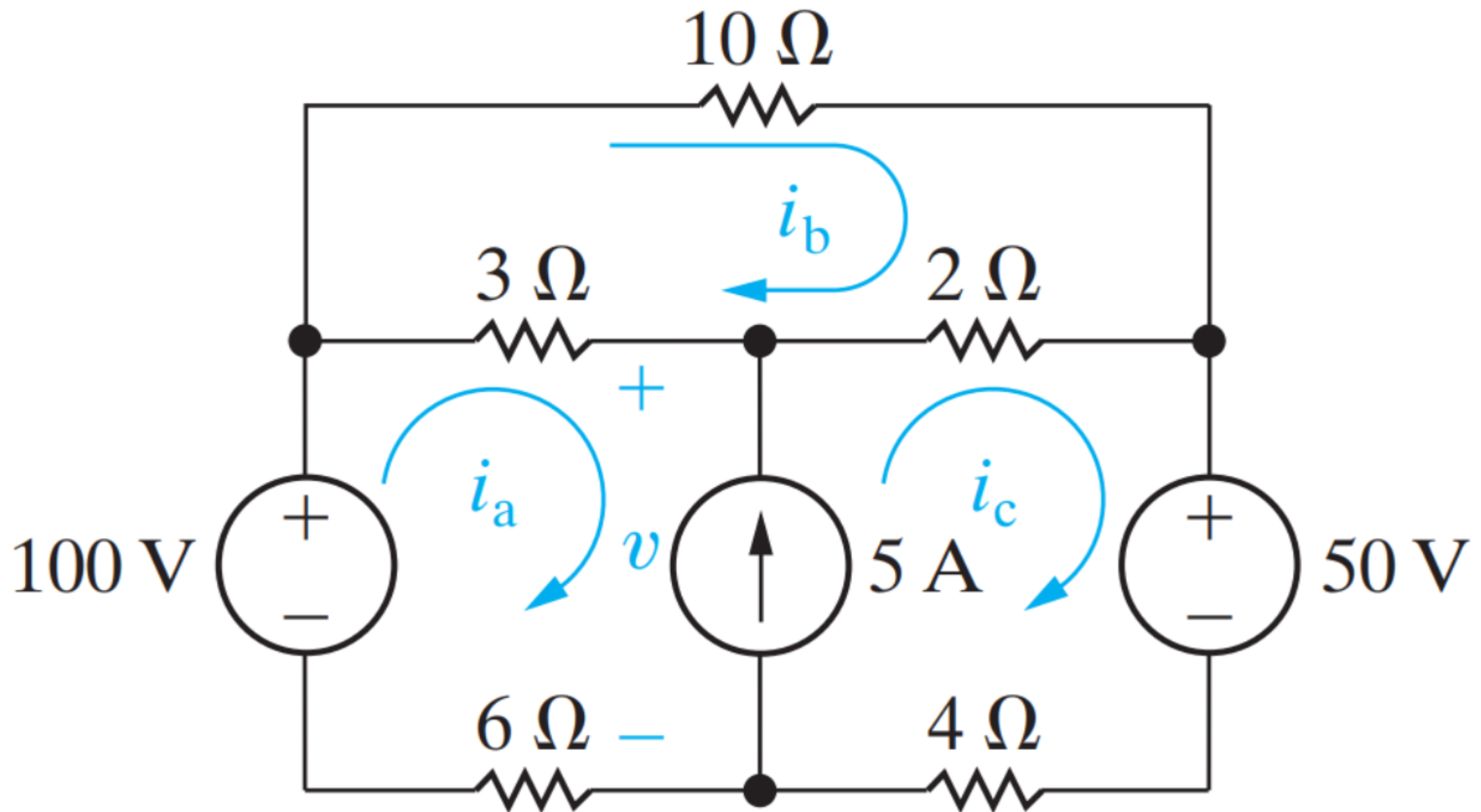


Supermesh Constraint Equation

Giannacco

In a Supermesh circuit analysis problem, a constraint equation can be used to match the number of equations with the number of unknowns in the system.



$$i_{Neg.} - i_{Pos.} = i$$

$$i_c - i_a = 5A$$

Adding a constraint to a system of equations ensures that i_c and i_a will have a 5-Amp difference.