


Voltage and Current Division

Giannacco

Voltage Division

$$v_j = iR_j = \frac{R_j}{R_{eq}} v$$

Series Connections Only

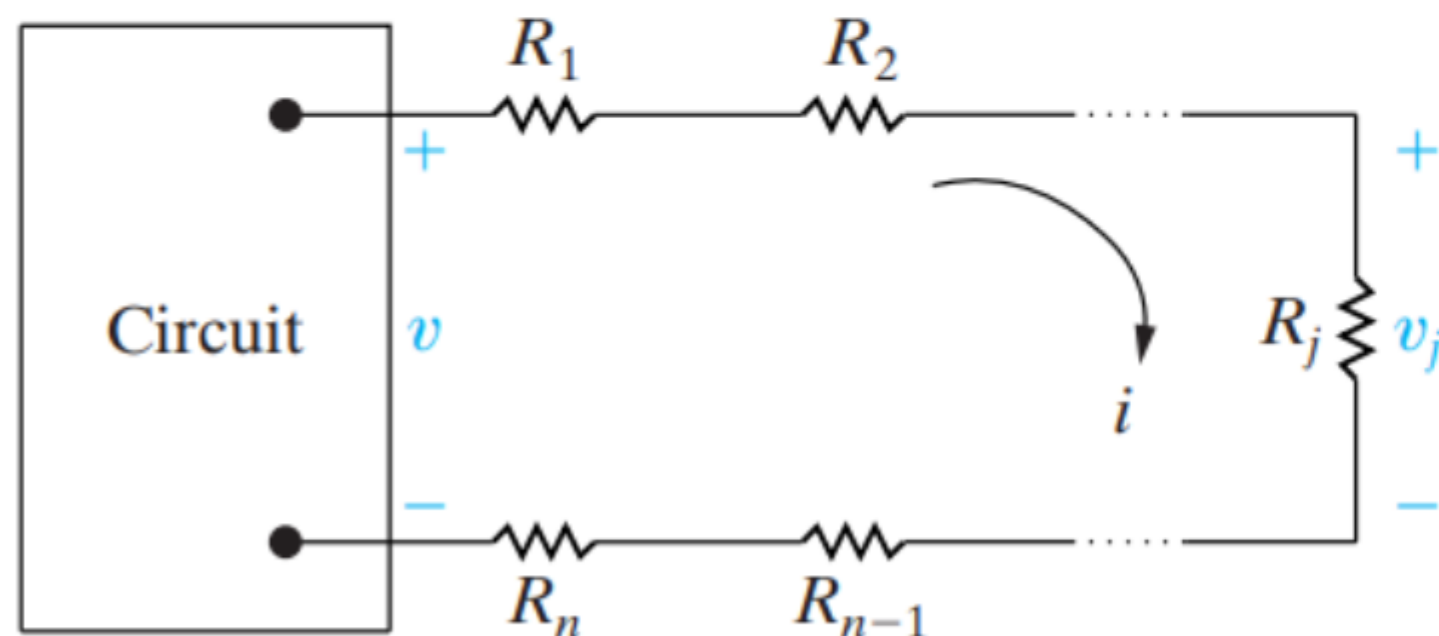


The Equivalent Resistance is calculated for Series Connections Only

Current Division

$$i_j = \frac{v}{R_j} = \frac{R_{eq}}{R_j} i$$

Parallel Connections Only

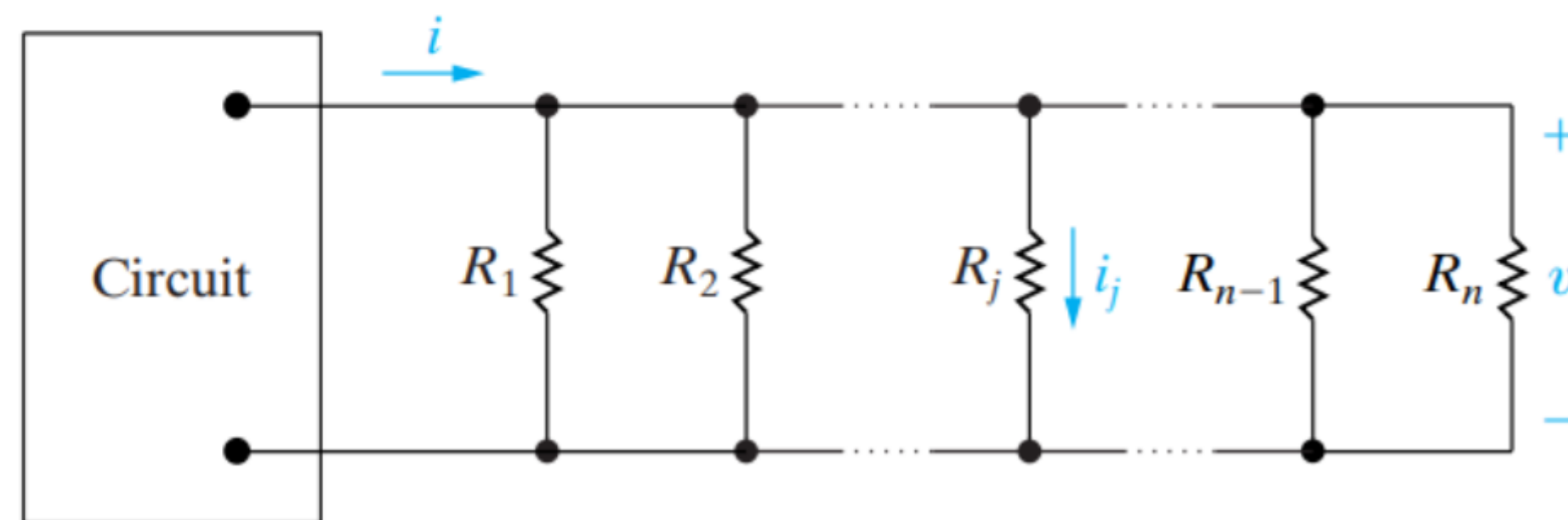

The Equivalent Resistance is calculated for Parallel Connections Only